

### 3.2 MiMo - model CPE

ponedeljek, 02. november 2020 17:37

Značilnosti :

- pomnilniška beseda

16 BITOV

- pomnilniški naslov

16 BITOV

- dolžina ukazov 16 ali 32 bitov (2 formata)

- Format 1 : (primer ADD R1,R2,R3 # R1<-R2+R3, R1=Dreg, R2=Sreg, R3=Treg)

- Format 2 : (primer LI R1, 100 # R1<-100)

- registri:

- 8x 16bitnih splošno namenskih registrov R0-R7

- operandi (pomnilniški dostopi) SAMO 16-BITNI

- pomnilniško preslikan vhod/izhod

- prekinitive

MiMo temelji na tem viru: <http://minnie.tuhs.org/Programs/UcodeCPU/index.html>

FORMAT1 :

Op.koda	Treg	Sreg	Dreg
7	3	3	3

ZAPIS V  
ZPISANIU

ADD

R1, R2, R3

FORMAT2:

Op.koda	Treg	Sreg	Dreg
7	3	3	3
16 bitni tak. operand			
	16		

LI R1, 100 @ R1<100

F1 + TAK.OPER

### 3.2.1 Izvrševanje ukazov


ponedeljek, 02. november 2020 17:42

→ "FETCH": UČITAVANJE PREDZERKOV CIKEL


→ "EXECUTE": IZVRŠILNI CIKEL

→ "ELEMENTARNI KORAKI" nivo  
→ "VEĆ PERIODNA REALIZACIJA"

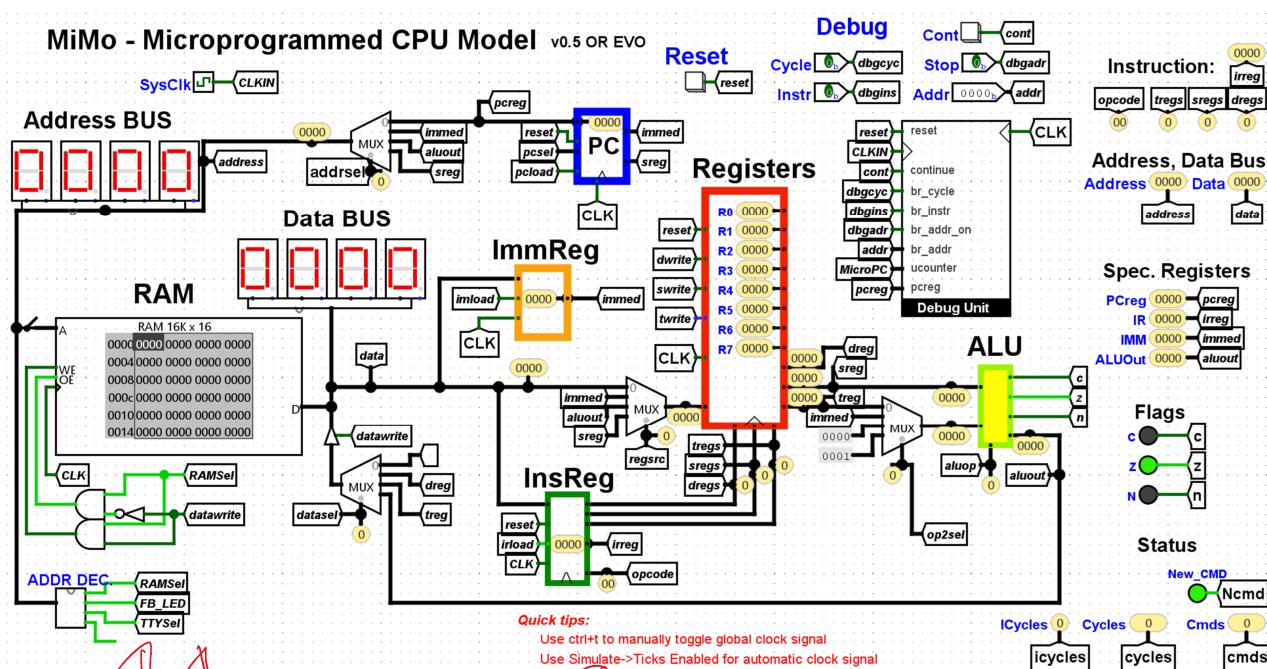
- BRANJE UVJAZA
- DEKODIRANJE (ANALIZA) UVJAZA
- PRENOŠ DIRENDOV
- IZVJEĐRA OPERACIJE (ALE)
- SHRANITEV REZULTAT
- OBNOVITEV PCje  
 $PC = PC + 1$




MOX-MULTIPLEXER

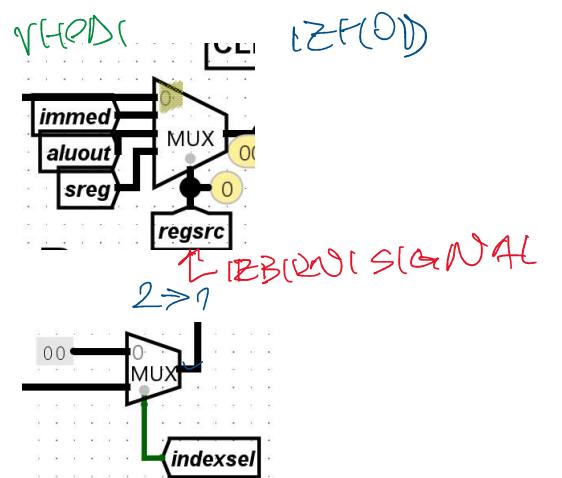


DEMUX-DEMULTIPLEXER

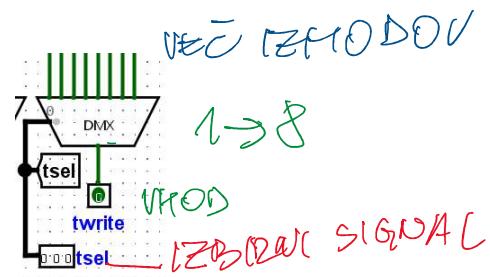


TUNELI (POVEZANE)

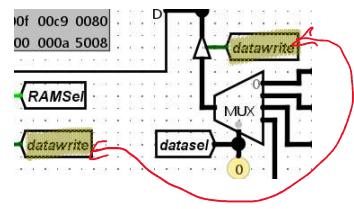

SPLITTER (RAZDELJUNIK)

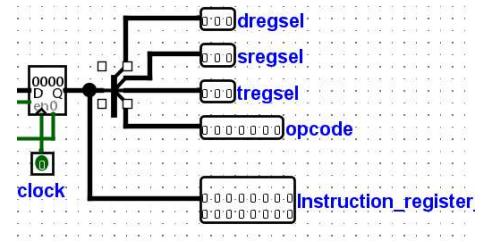
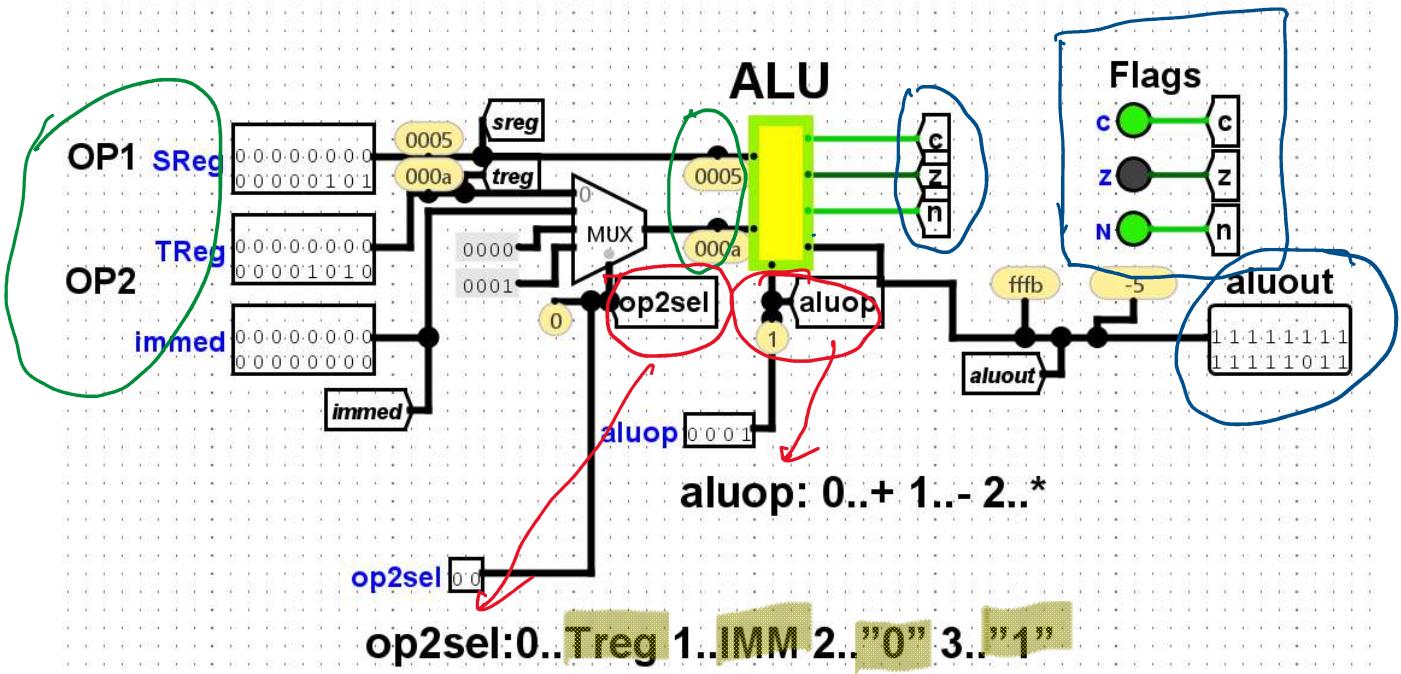
# MiMo - Microprogrammed CPU Model v0.5 OR



ALUOP : VRS ZA OPERACIJE


OP2SEL : DOLOČA 2. OPERAND

OP.KODA  
add Rd,Rs,Rt [0]  
Rd <- Rs + Rt  
ALUOP = 0  
OP2SEL = 0 ("TREG")

PC <- PC + 1


jnez Rs,immed (40)  
if Rs != 0, PC <- immed else PC <- PC + 2

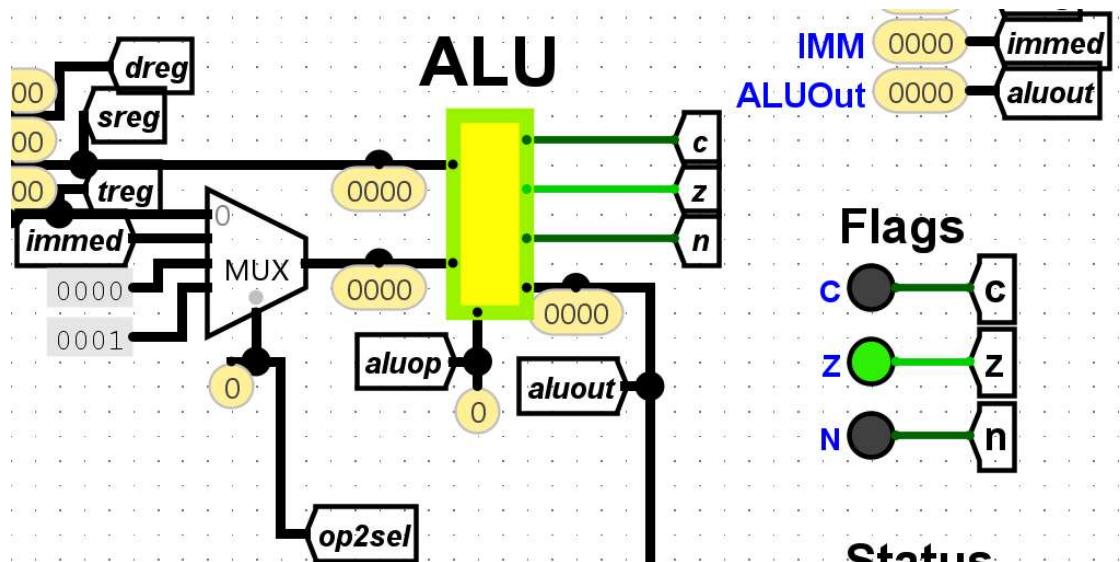ALUOP = 1  
OP2SEL = 2 ("0")  
R<sub>s</sub> = 0 = 2 2ASL.




## Registri

ponedeljak, 02. novembar 2020 17:46

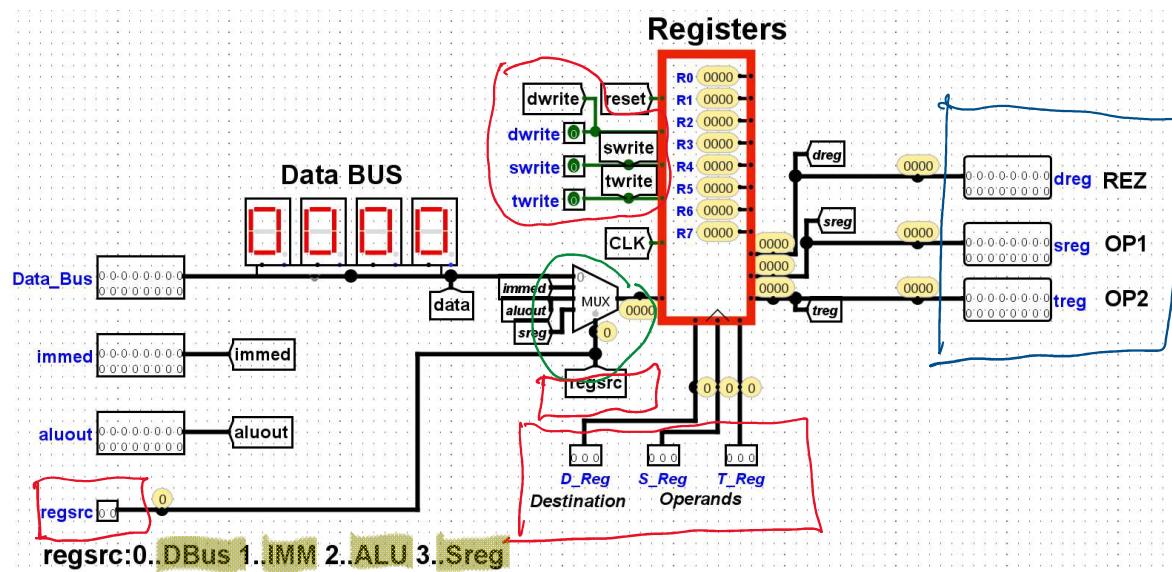



<i>add Rd,Rs,Rt (0)</i>	<i>move Rd,Rs (70)</i>	<i>li Rd,immed (63)</i>
<del>Rd = Rs + Rt</del>	<del>Rd = Rs</del>	<del>Rd = immed</del>
<del>REGSRC = 2</del>	<del>REGSRC = 3 (SREG)</del>	<del>REGSRC = 0 (DBUS)</del>
<del>DWRITE = 1</del>	<del>DWRITE = 1</del>	<del>DWRITE = 1</del>

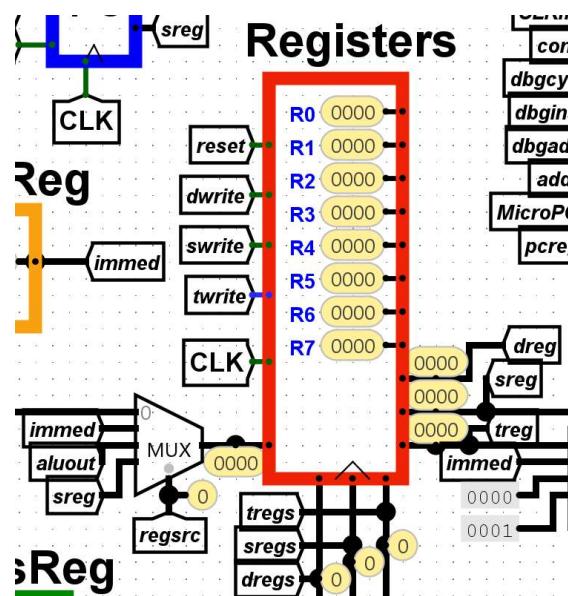
PC <- PC + 1      PC <- PC + 1      PC <- PC + 2



# PC - programski števec


ponedeljek, 02. november 2020 17:49

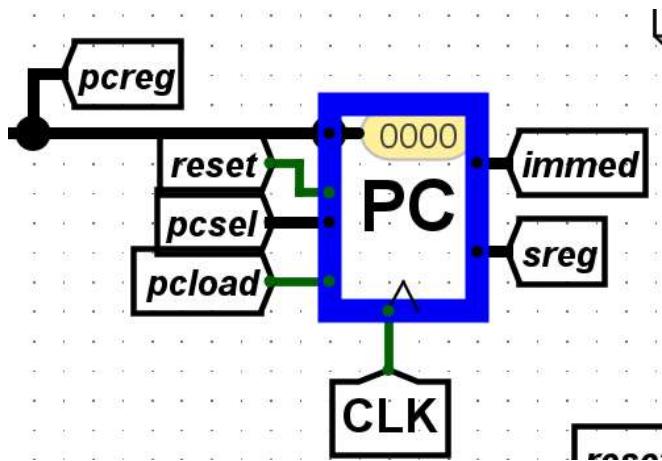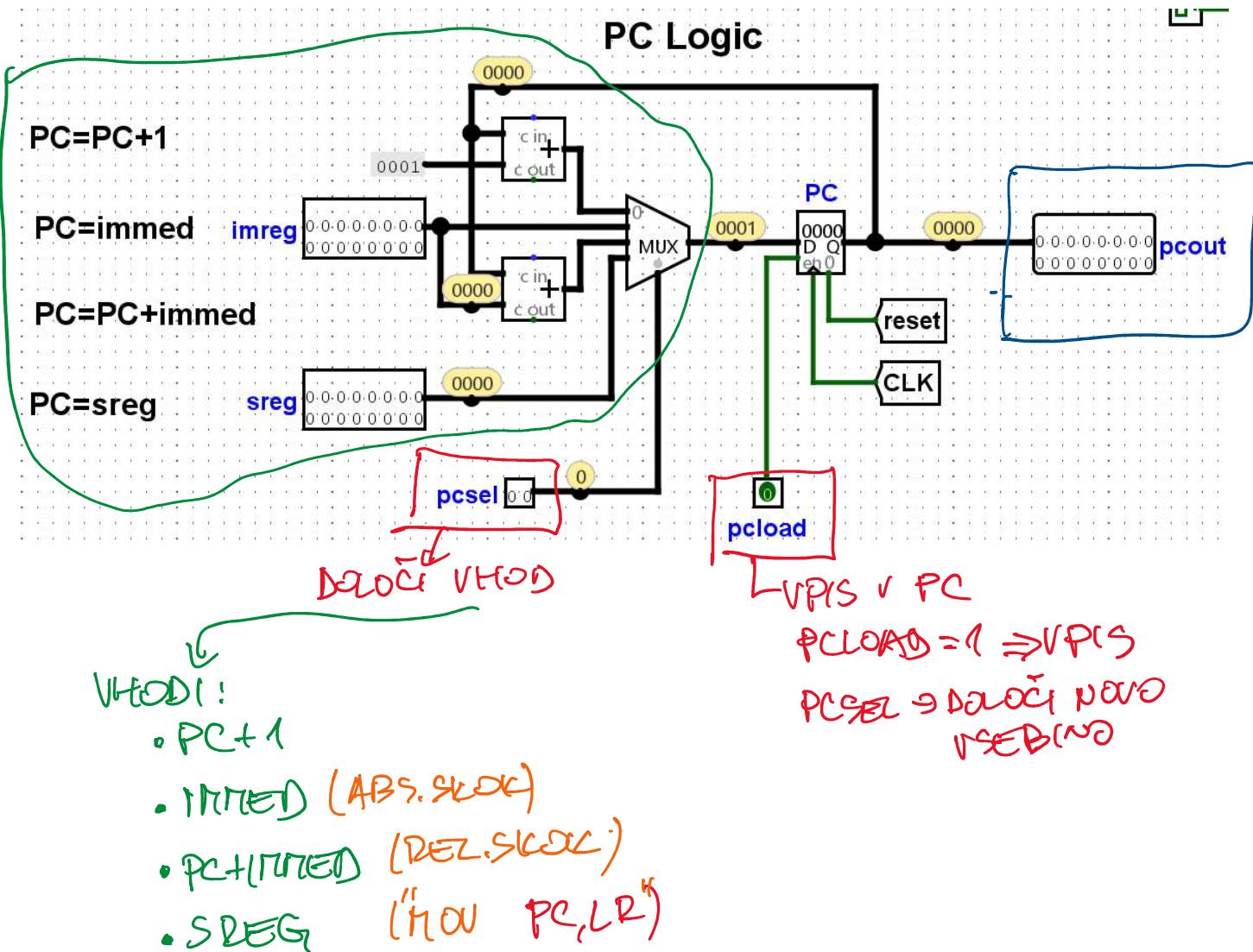

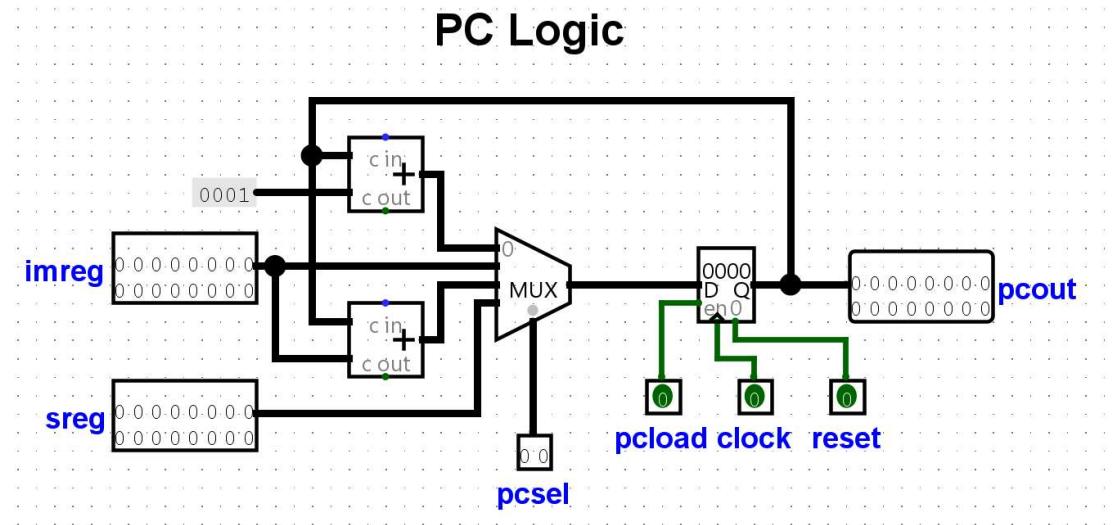

# IR - ukazni register

ponedeljek, 02. november 2020 17:50

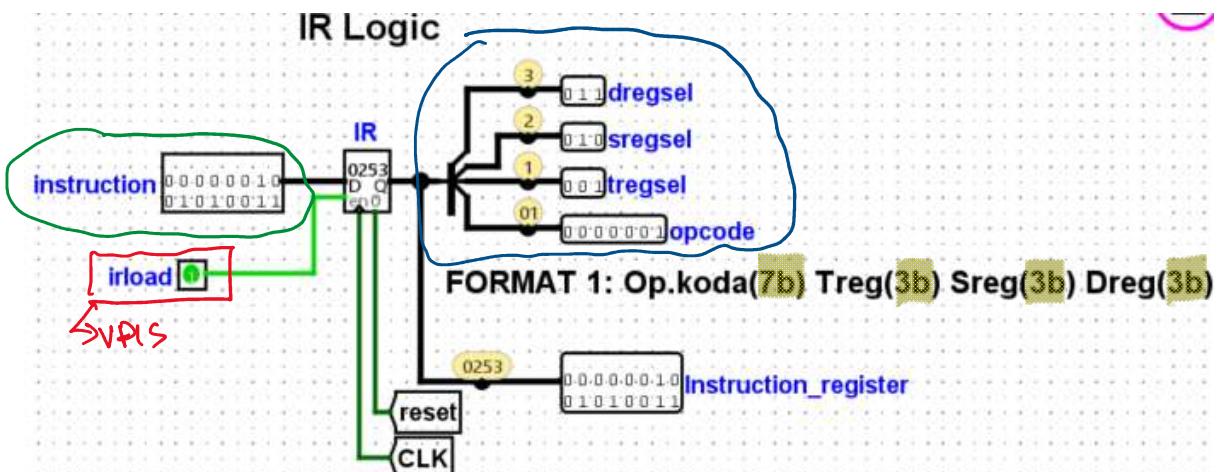

Zbirnik: add Rd,Rs,Rt

OP.KODA

d

sub Rd,Rs,Rt (1)

Rd <- Rs - Rt

▷ S ▷

SUB R3,R2,R1

PC <- PC + 1



add Rd,Rs,Rt (0)

Rd <- Rs + Rt

PC <- PC + 1

Op.koda	Treg	Sreg	Dreg
1	1	2	3

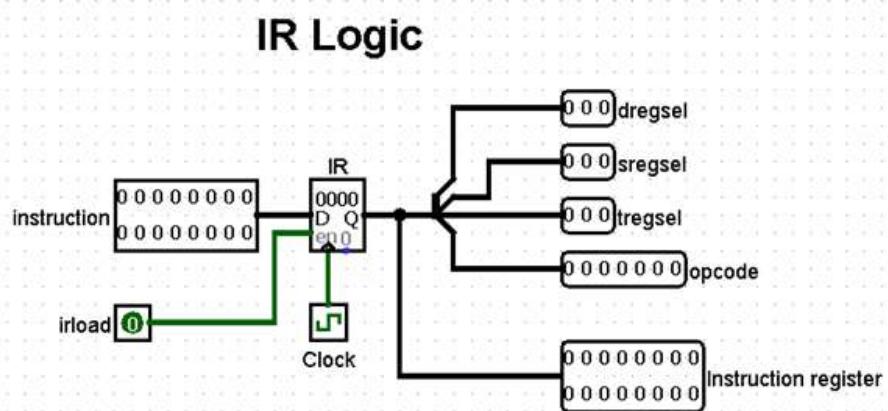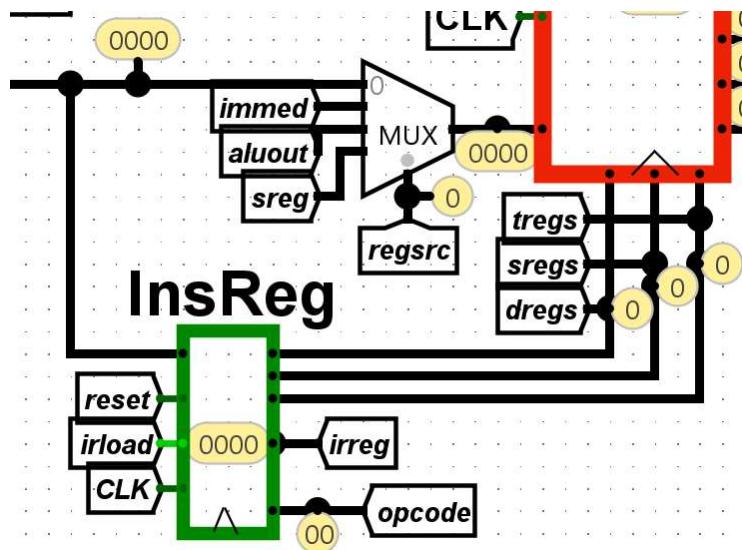
FETCH: • BRANJE UKAZA:  $IRLOAD = 1$   
 $(ADDRESSEL = PC)$



# IM - Takojšnji register

ponedeljak, 02. november 2020

17:51

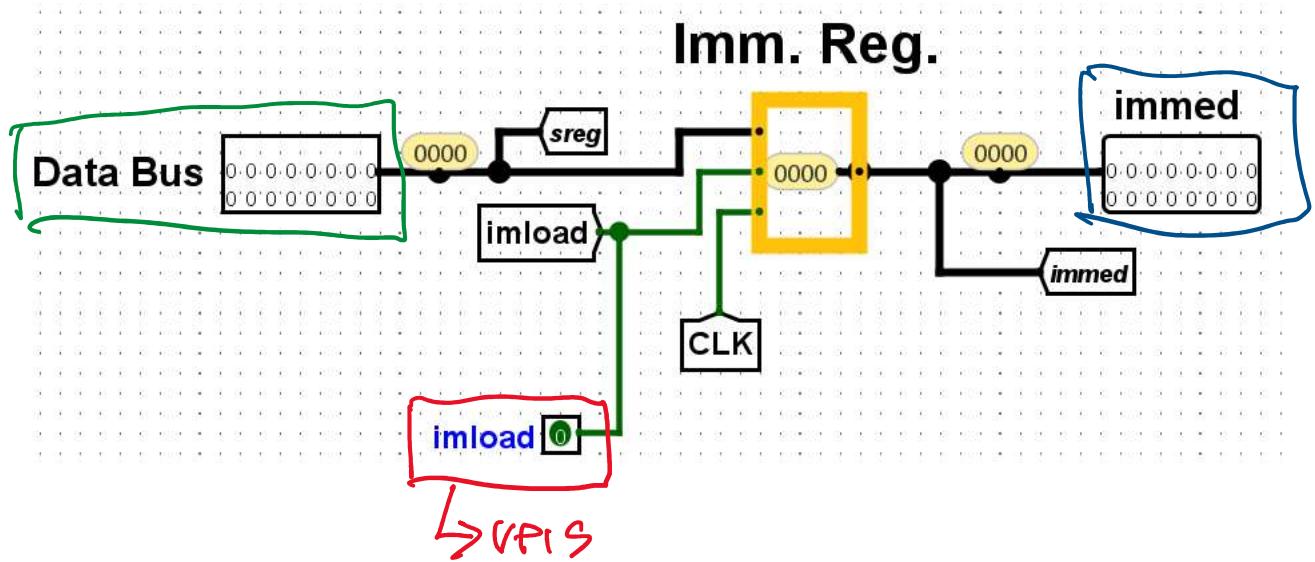

jnez Rs,immed (40)

if Rs != 0, PC <- immed else PC <- PC + 2

BOAUSKE TAKI D PETRANADA:

IMLD4D = 1

(POMNOVIMO TAKI.DP.)

li Rd,immed (63)


Rd <- immed


PC <- PC + 2


TAKI.DP → REG<sub>1</sub>.

IMLD4D = 0

(VPI5 IN REGISTER  
DIRECT NO)

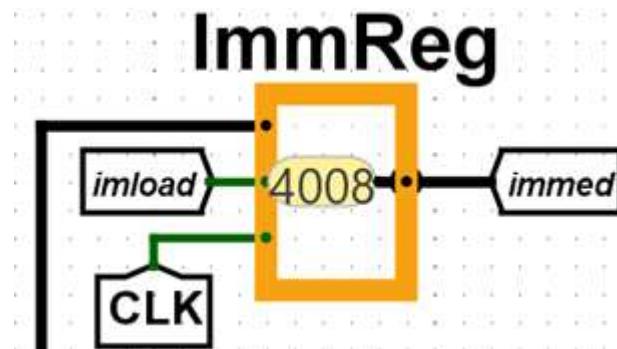

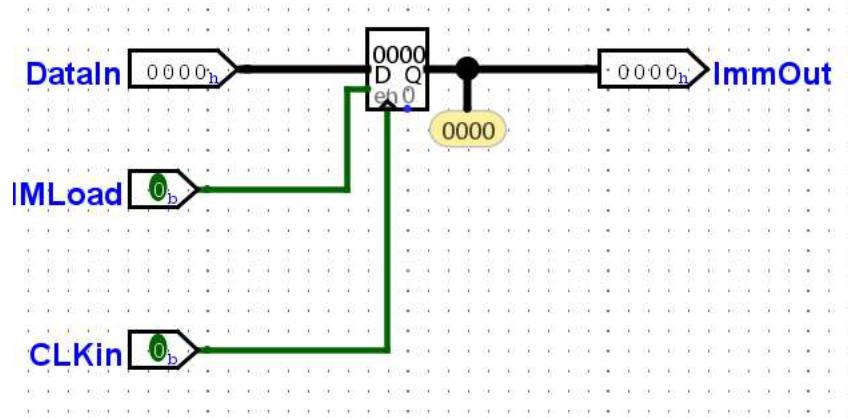

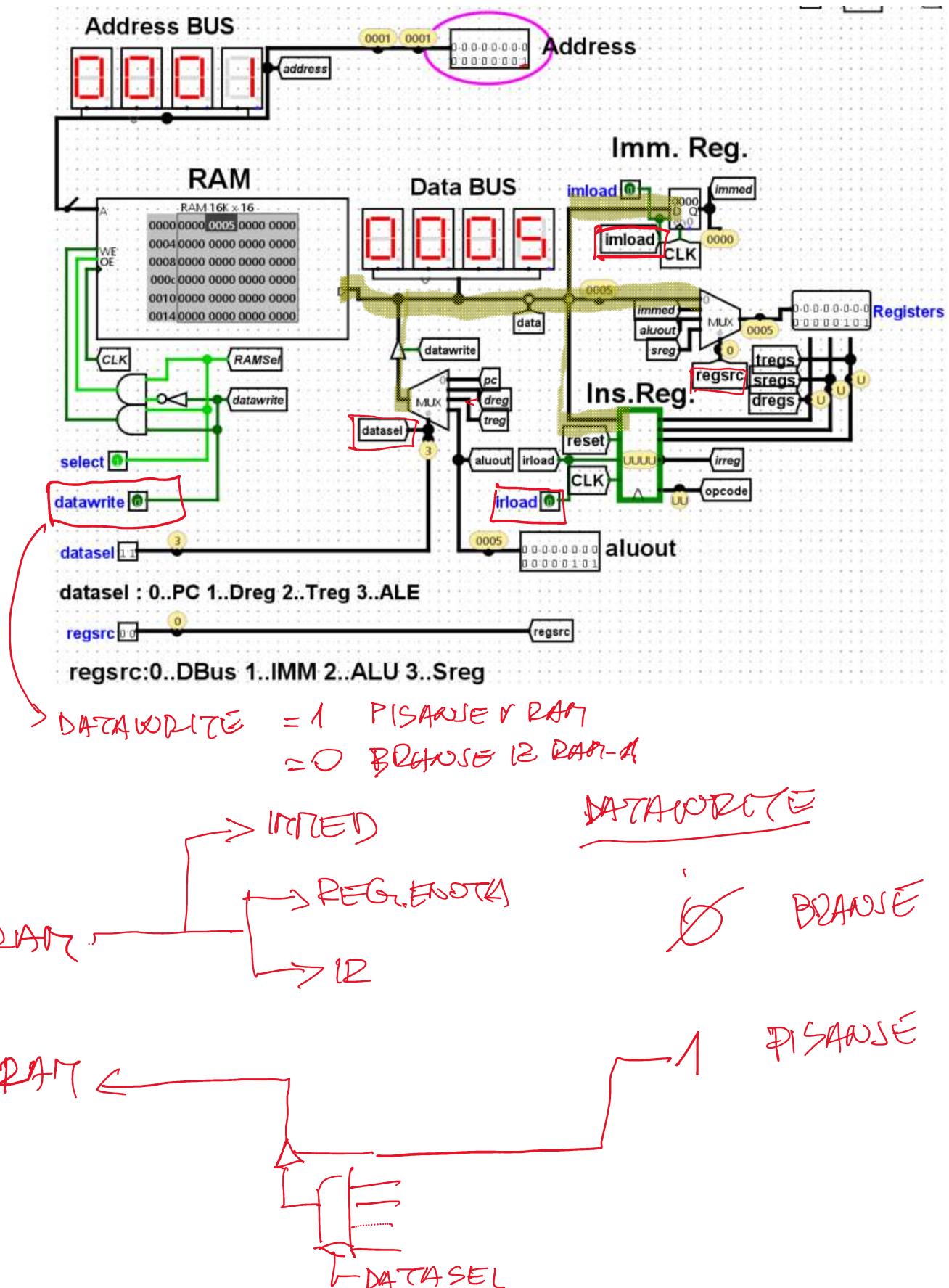

*sw Rd,immed (65)*

M[immed] <- Rd

PC <- PC + 2

BRANJE UZ RAM-A


DATAWRITE=1  
DATASEL = DREG  
ADDRESSL = (M7E0)

DATAWRITE=0  
ADR - NASLOV

# Naslovno vodilo

ponedeljek, 02. november 2020

17:54

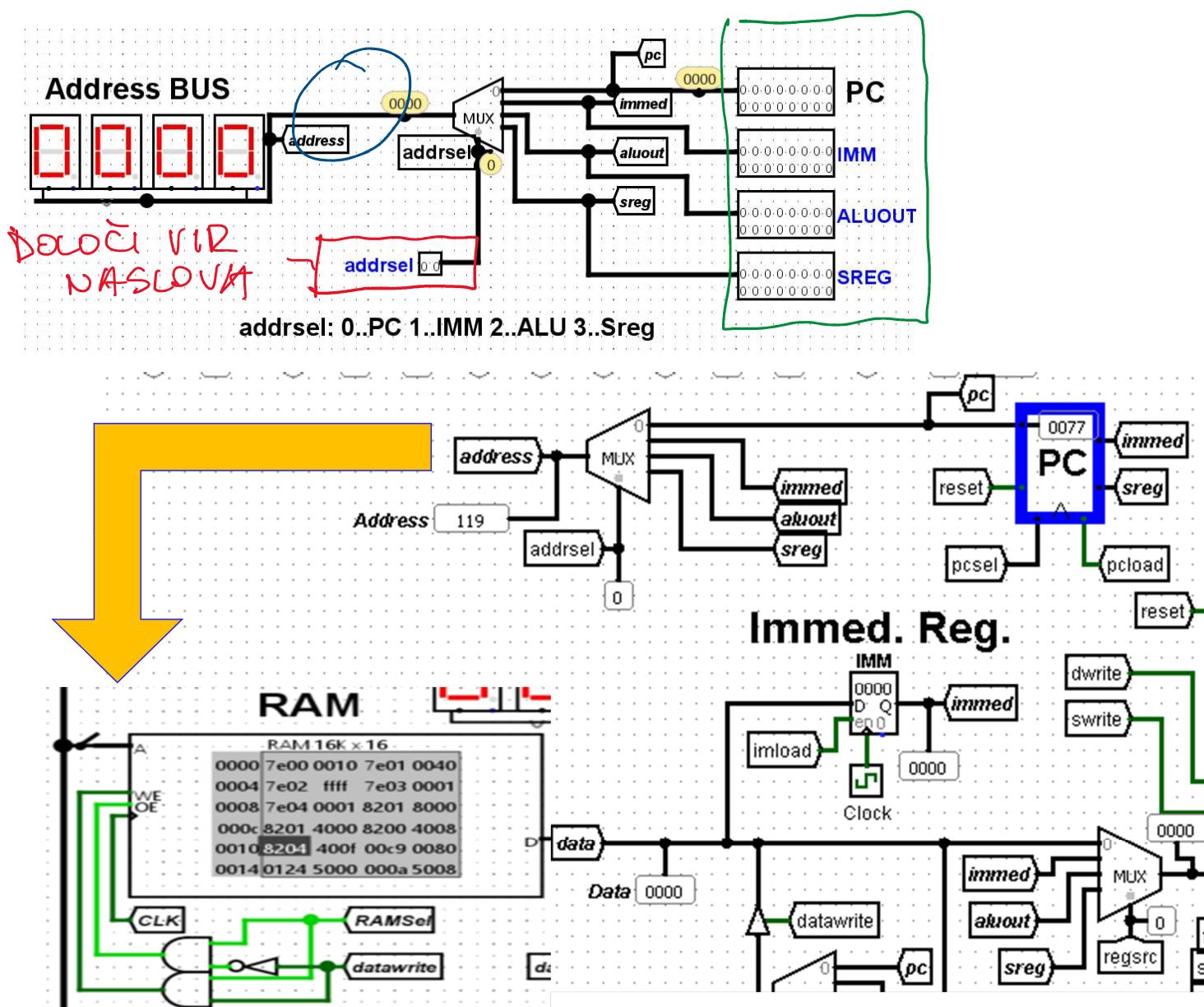

# ADDSEL

IMMED (1)

*sw Rd,immed (65)*

$M[\text{immed}] \leftarrow \text{Rd}$

$\text{PC} \leftarrow \text{PC} + 2$

ALUOUT (2)

*lwi Rd,Rs,immed (66)*

$\text{Rd} \leftarrow M[\text{Rs+immed}]$

$\text{PC} \leftarrow \text{PC} + 2$

ALUOUT (2)

*lwri Rd,Rs,Rt (73)*

$\text{Rd} \leftarrow M[\text{Rs+Rt}]$


$\text{PC} \leftarrow \text{PC} + 1$

# RAM pomnilnik

ponedeljek, 02. november 2020

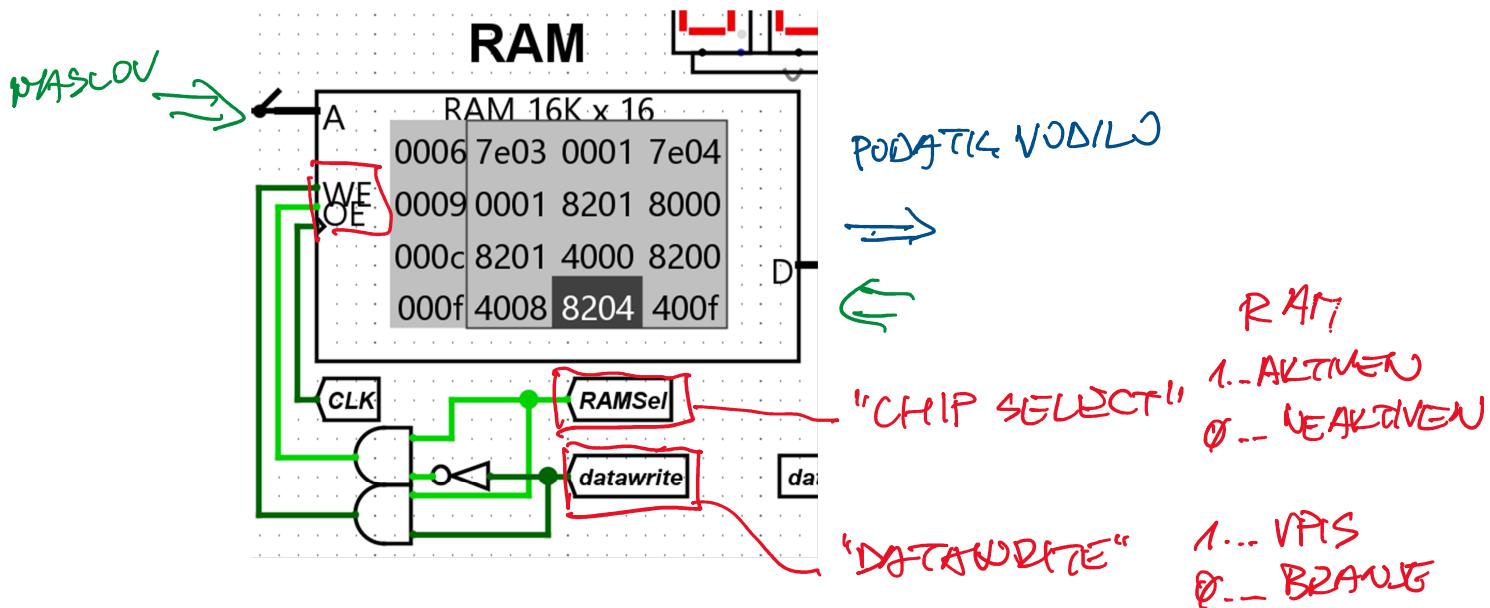17:54

P47: WE - WRITE ENABLE (PISANJE)  
OE - OUTPUT ENABLE (IZDRAZJE)



NEODPOLNO

NASLOVNO DEKODIRANJE



- 00 RAM
- 01 FB-LED
- 10 TTY
- 11 PROST

PODOLNI

0 - 16383


16384 - 32767

32768 -

## ||||| Izbera čipa (CS)

- Kako priključimo dve (ali več) naprav na vodilo?

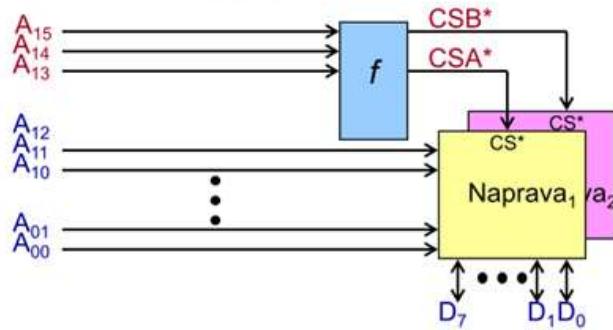
- Naenkrat mora biti izbran samo en čip (ali nobeden)
- Za izbiro uporabimo naslednje signale:
  - R/W\*, Naslov( $A_0$ - $A_{15}$ )
- Uporabni so biti, ki niso povezani na naslovne signale naprav ( $A_{15}$ - $A_{13}$ )
- CSA\* in CSB\* sta torej funkciji  $A_{15}$ - $A_{13}$ .



# FB - FrameBuffer


ponedeljek, 02. november 2020 17:55

## Frame Buffer LED 16x16

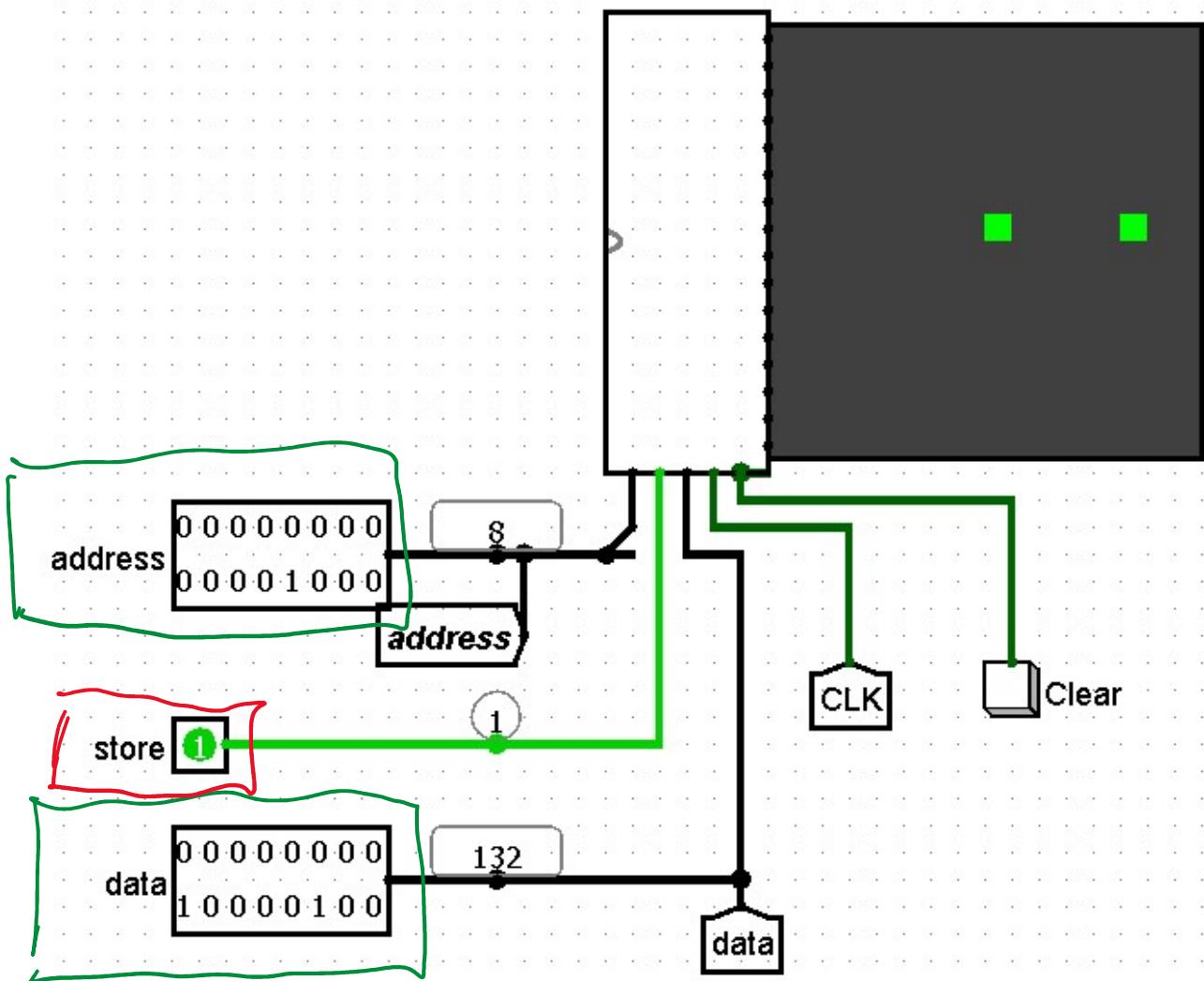


# TTY - Serijski terminal


ponedeljek, 02. novembar 2020 17:56

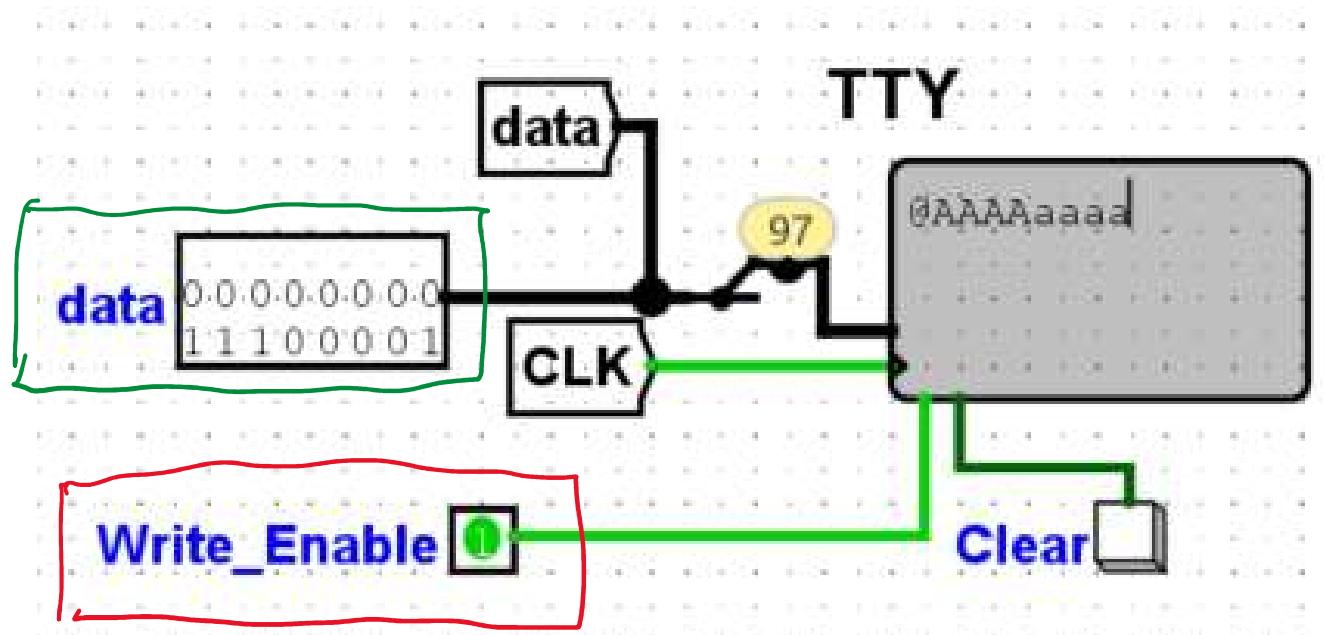

# Debug enota


ponedeljek, 24. oktober 2022 17:49

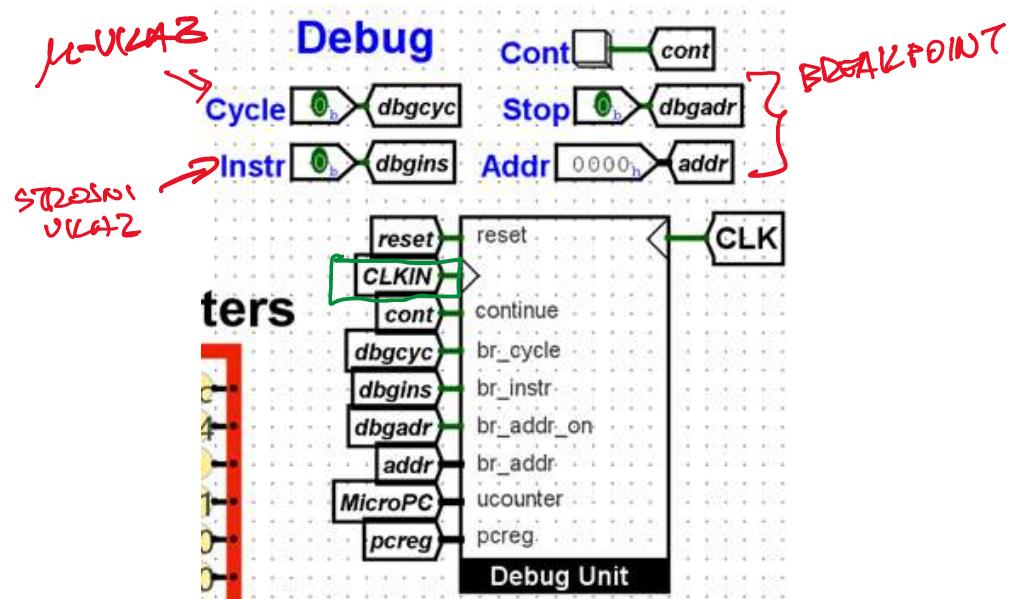

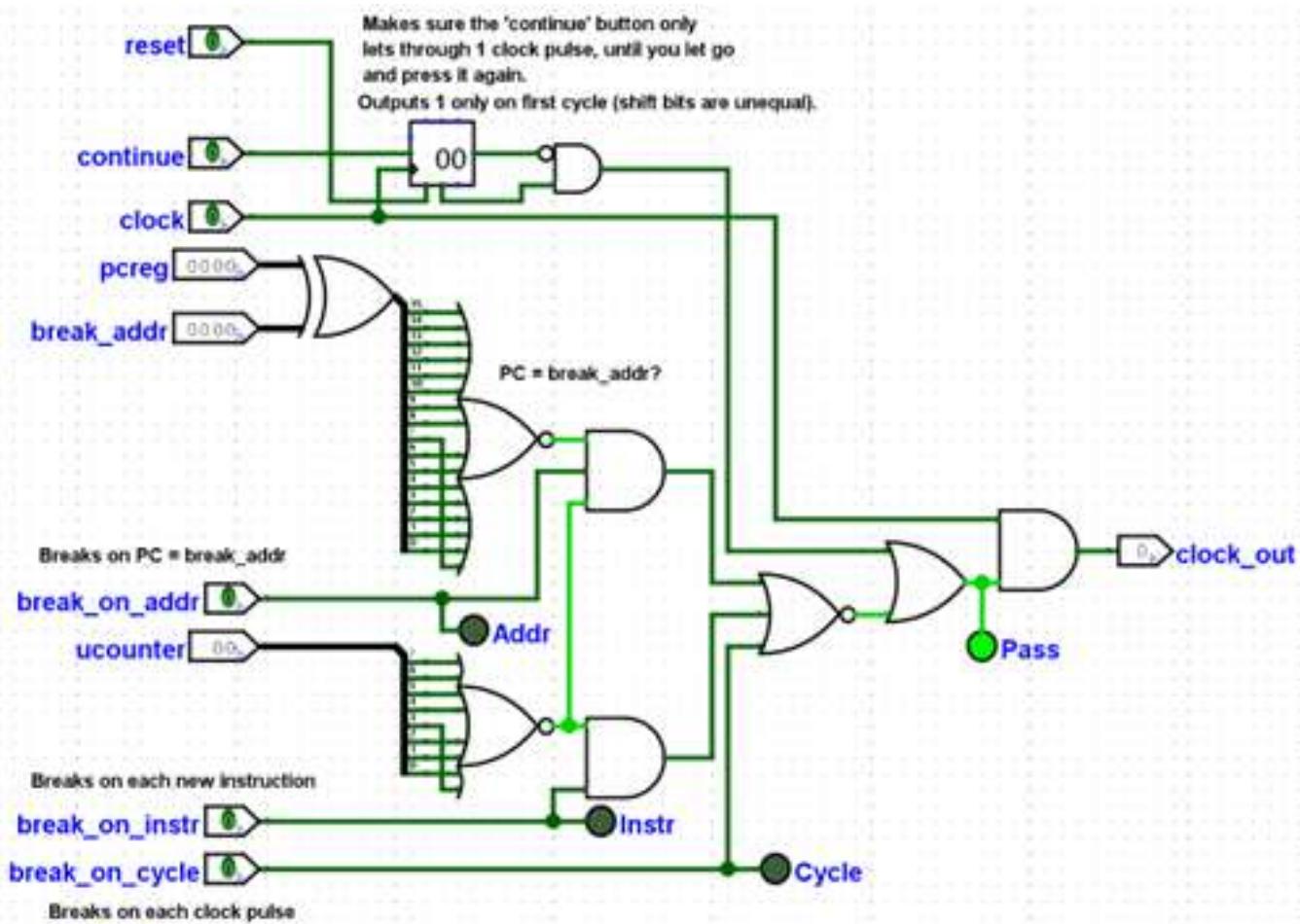

### 3.2.3 Kontrola enota

ponedeljek, 02. november 2020 17:57

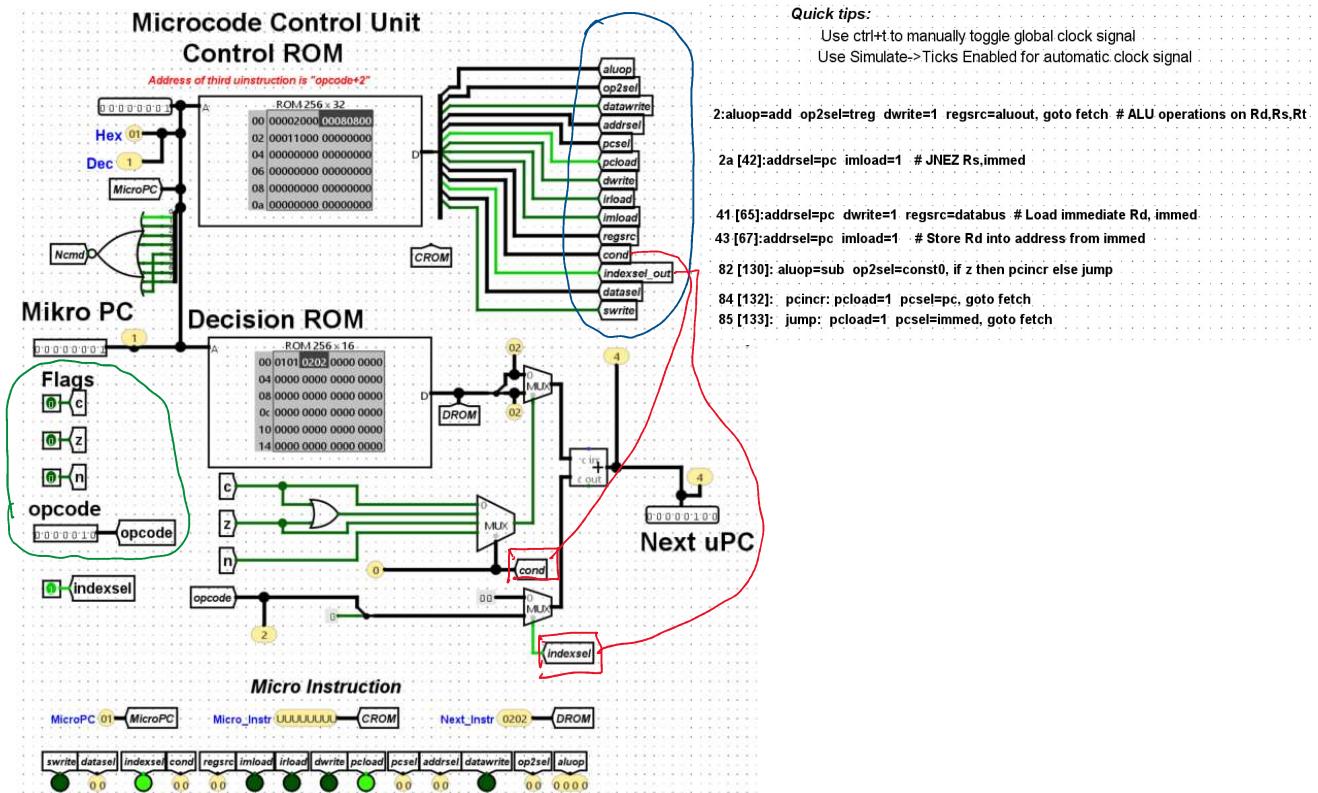


KE : SKRBI ZA IZVEDBO UKAZOV

LVSATI UKAZO IZVEDE PO VSEM ELEMENTARNIM KORAKOM

ELEMENTARNI KORAK = 1 μ-UKAZ


MORA DOLOCITI :

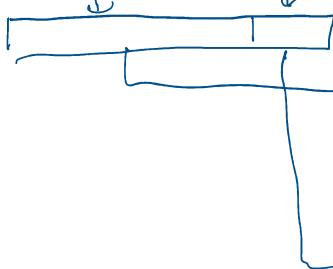- STANJE KONTROL-SIGNALOV
- NASLEDNJI μ-UKAZ



OPK	Opis	Skupna za vse ukaze	Z uprave
00: 00002000 0101	# fetch:addrsel=pc imload=1		
01: 00080000 0202	# pcload=1 pcesel=pc, opcode_jump		
02: 00011000 0000	# 0: aluop=add op2sel=treg dwrite=1 regsrc=aluout, goto fetch	add Rd,Rs,Rt (0)	Rd <= Rs + Rt
2a: 00004000 8282	# 40: addrsel=pc imload=1		
41: 00000000 8484	# 63: addrsel=pc dwrite=1 regsrc=databus, goto pcincr		
43: 00000000 8383	# 65: addrsel=pc imload=1		
82: 00004000 8283	# aluop=sub op2sel=const0, if z then pcincr else jump	jnez Rs,immed (40)	if Rs != 0, PC <= immed else PC <= PC + 2
83: 00100000 8484	# addrsel=immed datawrite=1 dataset=dreg, goto pcincr		
84: 00000000 0000	# pcincr: pcload=1 pcesel=pc, goto fetch		
85: 00000000 0000	# jump: pcload=1 pcesel=immed, goto fetch		


### Microcode Control Unit

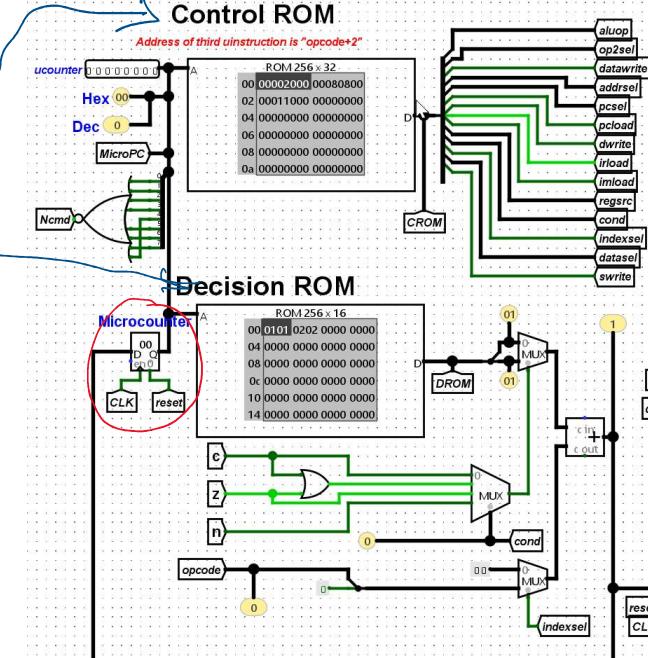

SESTAVLA KE :

cestava ke:

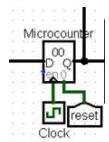
- $\mu$ -PC  $\rightarrow$  določa naslov  $\mu$ -ukaza  
fukro



## • 2 ROM POMNOVNika

32-BITNI "CONTROL ROM"

lisebne sezone kontrolnih signalov

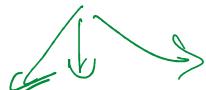

swrite	datasel	indexsel	cond	regsrc	imload	irload	dwrite	pcload	pcsel	addresel	datawrite	op2sel	aluop
00	00	00	00	00	00	00	00	00	00	00	00	00	0000

16-BITNI "DECISION ROM"

l določa naslov nasl.  $\mu$ -ukaza

Primer:

T F  
(5, 5) - brez p. skok

(5, 4) - T: 8 | F: 8

TRUE:  $\mu$ PC = 5 FALSE:  $\mu$ PC = 4

NASL. NAL.  $\mu$ -UKAZA

## PRIMERI DELOVANJA KE:


### ① "OPCODE JUMP"

- INDEXSEL = 1 ( $\mu$ PC = 1)
- NASL. NAL.  $\mu$ -UKAZA

2 + OP. KODA

② "IF Z THEN PC INC  
ELSE JUMP"


- COND = Z
- DECISION ROM

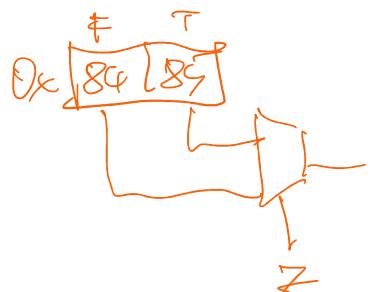

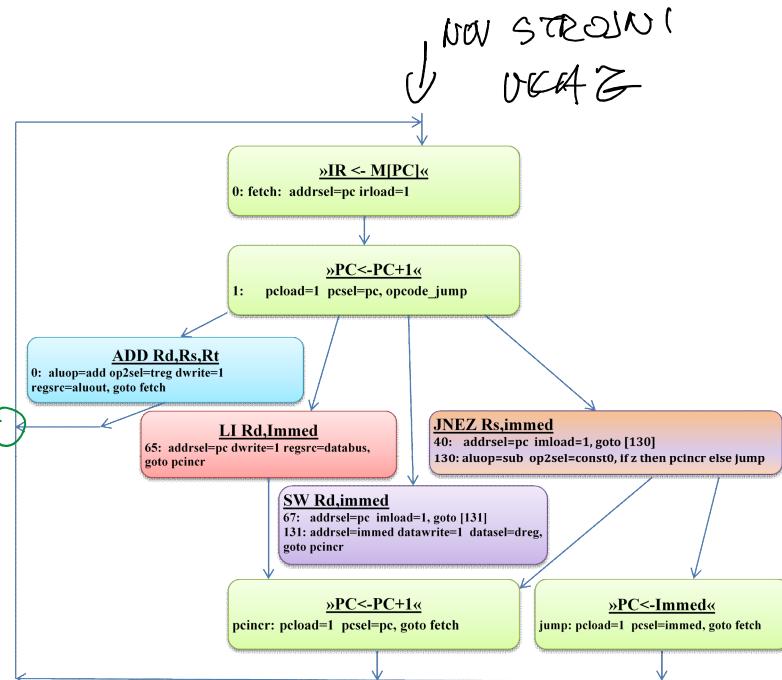
# Diagram prehajanja stanja

ponedeljek 09. novembar 2020 20:59

**OBICAJEN KONCEPT  
OPISUVAANJA JE  
RAZVODNA IZGODA  
UKAZOV  
OSNOVA ZA OPTIMIZACIJU**



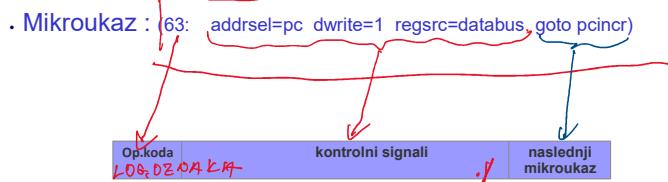

DODAN VZETI CE

NASLEDNJI µ-UKAZ :

- "PRAZNO" ---  $\mu$ PC+1
- GOTO OZNAKA --- V KOSTICI "OZNAKA"
- IF PEGOS THEN OZNAKA1  
| ELSE OZNAKA2
- IF PEGOS THEN OZNAKA . - SICER  $\mu$ PC+1
- OPCODE\_JMP

kontr. signal	opisna vrednost	enota
aluop	add, sub, mul, div, rem, and, or, xor, nand, nor, not, lsl, lsr, asr, rol, ror	ALE
op2sel	treg, immmed, const0, const1	ALE
addrsel	pc, immmed, aluout, sreg	nasl. vodilo
pcsel	pc, immmed, pcimmmed, sreg	PC
regsrc	databus, immmed, aluout, sreg	registri
cond	c, corz, z, n	kontr. enota

datoteka basic\_microcode.def PREGOVO

```

fetch: address=pc irload=1          # Address=PC, Load IR register
       pload=1 pcel=pc, opcode_jump  # PC=PC+1, jump to 2+OPC

# ALU operation '+' on Rd,Rs,Rt
0:   aluop=add op2sel=treg dwrite=1 regsrc=aluout, goto fetch

# JNEZ Rs,immmed
40:  address=pc imload=1           # JNEZ
     aluop=sub op2sel=const0, if z then pcincr else jump

# li Rd,Immmed
63:  address=pc dwrite=1 regsrc=databus, goto pcincr

# Rd->M[immmed]
65:  address=pc imload=1           # Rd->M[immmed]
     address=immmed dwrite=1 dataset=dreg, goto pcincr

pcincr: pload=1 pcel=pc, goto fetch
jump:  pload=1 pcel=immmed, goto fetch



```


. RAZPORED µ-UKAZOV V ROM FORTNIKU

Naslov	Vsebina
0	BRANJE UKAZA
1	PC<PC+1, OPCODE_JMP
2-129	OPCODE       0: PRVI µ-UKAZ 1 24 VSAC       1: STOSAC µ-UKAZ (128)
130+ 0x82+	VSI OSTALI µ-UKAZI

MICRO\_ASSEMBLER.EXE  
IME.DEP  
.PL

→ UCONTROL.ROM  
→ VDECISION.ROM

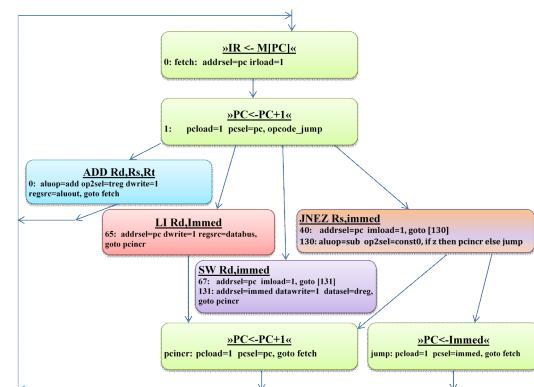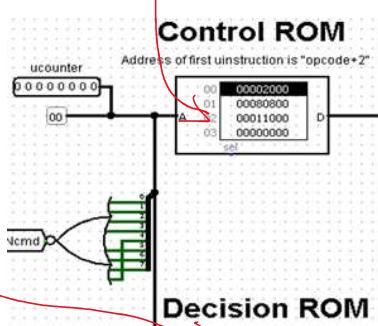

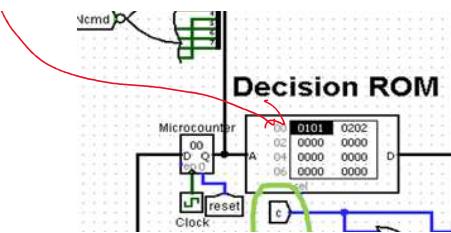

EVORNO KOD

datoteka basic\_microcode.def

```

fetch: addrsel=pc irload=1          # Address=PC, Load IR register
      pload=1 psel=pc opcode_jump    # PC=PC+1, Jump to 2+OPC
      
```

```

# ALU operation '+' on Rd,Rs,Rt
0: aluop=add op2sel=treg dwrite=1 regsrc=aluout, goto fetch
      
```

```

# JNEZ Rs.immed
40: addrsel=pc imload=1           # if z then pcincr else jump
      aluop=sub op2sel=const0
      
```

```

# li Rd,Immed
63: addrsel=pc dwrite=1 regsrc=database, goto pcincr
      
```

```

# Rd->M[immed]
65: addrsel=pc imload=1           # addrsel=immed datawrite=1 dataset=dreg, goto pcincr
      addrsel=immed
      
```

pcincr: pload=1 psel=pc, goto fetch

jump: pload=1 psel=immed, goto fetch

se prevede v index sel pload

00: 00002000 0101	# fetch: addrsel=pc irload=1
01: 00080800 0202	# pload=1 psel=pc opcode_jump
02: 00011000 0000	# 0: aluop=add op2sel=treg dwrite=1 regsrc=aluout,
23: 00040000 8282	# 40: addrsel=pc imload=1
41: 00001000 8484	# 63: addrsel=pc dwrite=1 regsrc=database,
43: 00004000 8383	# 65: addrsel=pc imload=1
82: 00040021 8485	# aluop=sub op2sel=const0,
83: 00100000 8484	# addrsel=immed datawrite=1 dataset=dreg,
84: 00000800 0000	# pcincr: pload=1 psel=pc,
85: 00000a00 0000	# jump: pload=1 psel=immed,

```

      goto fetch
      (goto 82)
      goto pcincr
      (goto 83)
      if z then pcincr else jump
      goto pcincr
      goto fetch
      goto fetch
      
```

post uvjeti

ostali

$\mu$ -ROM  
control  
ROM  
DECISION  
ROM

### 3.2.5 Zbirnik

ponedeljek, 09. november 2020 22:01


#### ■ Primer (testni):

```

main: li r0, 0           # r0 is the running sum
      li r1, 100          # r1 is the counter
      li r2, -1           # Used to decrement r1
loop: add r0, r0, r1    # r0= r0 + r1
      add r1, r1, r2    # r1--
      jnez r1, loop     # loop if r1 != 0
      sw r0, 256         # Save the result
inf:  jnez r2, inf      # loop if r1 != 0 -> loop forever
  
```

PROGRAM

POROČILO:

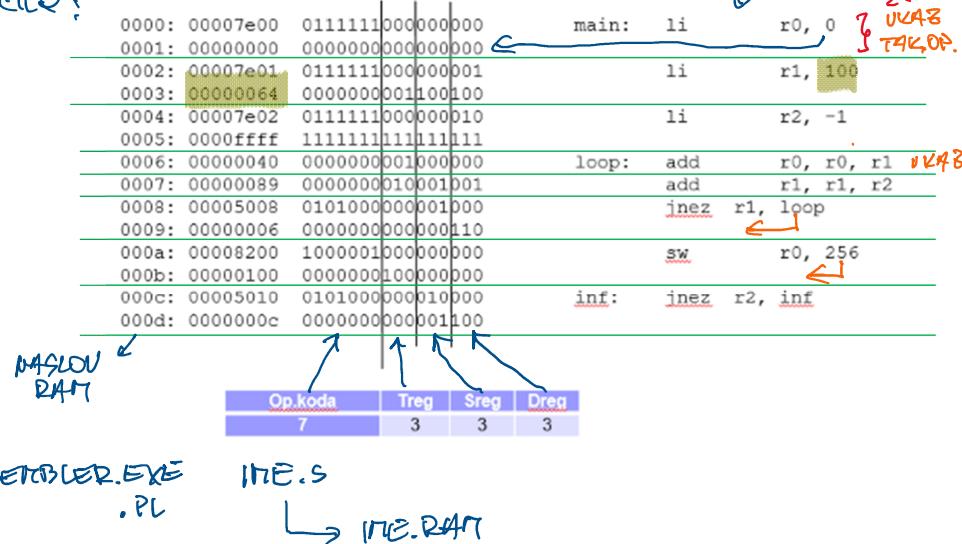

list\_of\_instructions.txt (distribucija) :

rdeče: trenutno že implementirani ukazi v modelu MiMo.

- add Rd,Rs,Rt (0)       $Rd \leftarrow Rs + Rt, PC \leftarrow PC + 1$
- sub Rd,Rs,Rt (1)       $Rd \leftarrow Rs - Rt, PC \leftarrow PC + 1$       ↳ LAB
- ...
- jeqz Rs,immed (39)      if  $Rs == 0$ ,  $PC \leftarrow immed$  else  $PC \leftarrow PC + 2$
- jnez Rs,immed (40)      if  $Rs \neq 0$ ,  $PC \leftarrow immed$  else  $PC \leftarrow PC + 2$
- ...
- beq Rs,Rt,immed (46)      if  $Rs == Rt$ ,  $PC \leftarrow PC + immed$  else  $PC \leftarrow PC + 2$
- bne Rs,Rt,immed (47)      if  $Rs \neq Rt$ ,  $PC \leftarrow PC + immed$  else  $PC \leftarrow PC + 2$
- ...
- li Rd,immed (63)       $Rd \leftarrow immed, PC \leftarrow PC + 2$
- sw Rd,immed (65)       $M[immed] \leftarrow Rd, PC \leftarrow PC + 2$
- ...
- lw Rd,immed (64)       $Rd \leftarrow M[immed], PC \leftarrow PC + 2$
- lwi Rd,Rs,immed (66)       $Rd \leftarrow M[Rs+immed], PC \leftarrow PC + 2$
- swi Rd,Rs,immed (67)       $M[Rs+immed] \leftarrow Rd, PC \leftarrow PC + 2$

□ swi Rd.Rs.immed (67)     $M[Rs+immed] \leftarrow Rd$ ,  $PC \leftarrow PC + 2$

SINTAKSIS  
DP-LODAR  
OPS

Enota ?	KE	KE	ALU	ALU	IMM	IR	PC	PC	NASL.VOD.	
JNEZ Rs, IMMED	INDEXSEL	COND	ALUOP	OP2SEL	IMLOAD	IRLOAD	PCLOAD	PCSEL	ADDRSEL	MicroPC
# Address=PC, Load IR register						1			Pc (0)	0
# PC=PC+1, jump to 2+OP	1						1	0 (PC+1)		1
# Read Immediate operand -> IMRegister					1				Pc (0)	42
# ALU: Rs-0, If z then pcincr else jump	2 ("z")	1 (SUB)	2 (CONST0)						130	z=1
# Increment PC and goto new command;							1	0 (PC+4)	132	z=0
# Set address to immed and goto new command							1	1 (IMMED)	133	

Annotations from the handwritten notes:

- 1: PC selection (PC or PC+1)
- 2: ALU operation (SUB or CONST0)
- 3: PC increment (130 or 132)
- 4: Jump condition (z=1 or z=0)
- 5: New PC value (133)

Handwritten notes:

- 1: PC selection (PC or PC+1)
- 2: ALU operation (SUB or CONST0)
- 3: PC increment (130 or 132)
- 4: Jump condition (z=1 or z=0)
- 5: New PC value (133)

### 3.2.6 Mikropogramirana vs trdoozičena CPE

ponedeljek, 09. novembar 2020 22:01


#### Izhodišča:

- Diagram poteka
- Elementarni koraki

Z POSEOTITI

M-PROG R.!



+ FLEKSIBILNOST  
+ ENOSTAVNA

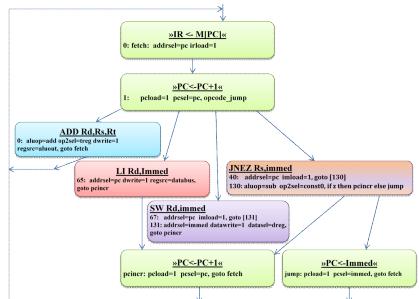


TRDOOŽIČENA ("HARD WIRED")  
+ HITROST  
- KOMPLEKSNOŠT

Elementarni koraki:  
 0 ... Branje ukaza -> IR  
 1 ... Format 2: branje operanda  
 Format 1: nop  
 2 ... Vse operacije:  
 □ ALE, skok, reg.write,  
 R/W from Mem

} FETCH  
} EXECUTE

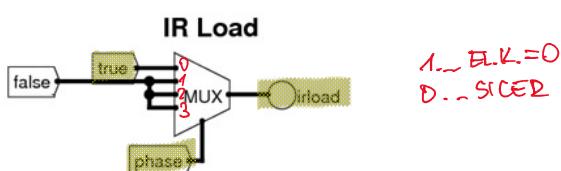
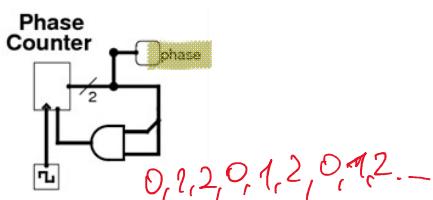



1. ~ E.L.K.=0  
D. ~ SICED

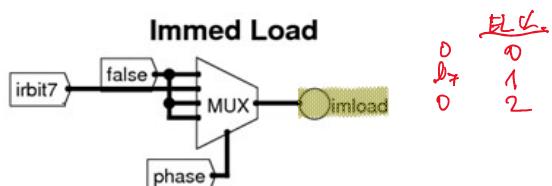

E.L.K.  
0 0 1 2

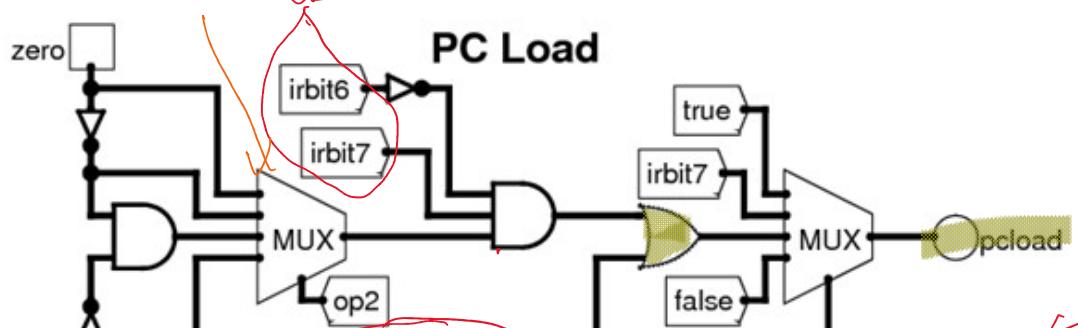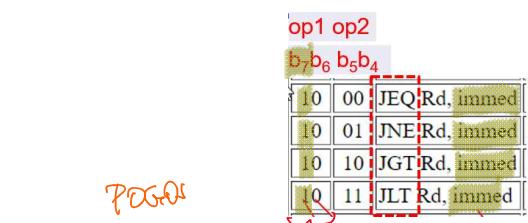irbit7:  
0 ... 8-bitni ukaz (1 bajt)  
1 ... 16-bitni ukaz (2 bajta)



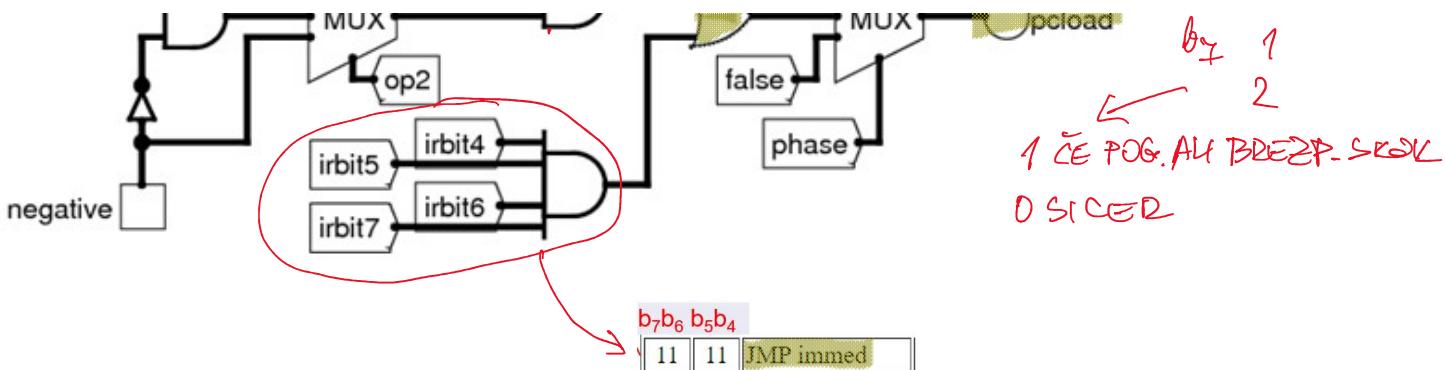

Podrobnejší opis - dodatno gradivo:  
<http://minnie.tuhs.org/CompArch/Tutes/week03.html>

